

# **MICROCONTROLLER - BASED**

**4 - DIGIT**

**8 – STAGE**

**SEQUENTIAL TIMER**

**(INPUT – LIMIT SWITCH)**

*Installation and Operating Manual*

## **CONTENTS**

<b>CHAPTER 1</b>	
GENERAL INFORMATION.....	3
<b>CHAPTER 2</b>	
SPECIFICATIONS.....	3
<b>CHAPTER 3</b>	
PRINCIPLE OF OPERATION.....	4
<b>CHAPTER 4</b>	
KEYBOARD SETTINGS.....	5
<b>CHAPTER 5</b>	
CONNECTION DIAGRAM.....	6

## **CHAPTER 1**

### **GENERAL INFORMATION:**

1. WHEN THE INSTRUMENT IS VIEWED FROM THE FRONT. THERE ARE 2 DISPLAY WINDOWS, WHICH ARE VISIBLE.

A. A 4 DIGIT DISPLAY WINDOW (TIMER VALUE)= **W-1**.

B. A 4 DIGIT DISPLAY WINDOW (STAGE NO) = **W-2**.

BELOW THE DISPLAY WINDOWS, THERE ARE EIGHT TUCTILE KEYS. THESE ARE

<b>SET KEY</b>	USED FOR SETTING THE SET POINTS FOR INDIVIDUAL RELAYS.
<b>F1 KEY</b>	NOT USED HERE.
<b>RST KEY</b>	TO RESET THE TIMER.
<b>ENT KEY</b>	FOR ADVANCING IN THE SET POINT MODE.
<b>ARROW KEYS</b>	TO SET THE DISPLAY.

## **CHAPTER 2**

### **SPECIFICATIONS:**

<b>MAINS SUPPLY</b>	90 - 260 VAC, 50 Hz.
<b>POWER CONSUMPTION</b>	LESS THAN 12 VA AT 230 VAC.
<b>SIGNAL INPUT</b>	LIMIT SWITCH
<b>CONTROL OUTPUT</b>	8 RELAY O/PS. (ONE RELAY FOR EACH STAGE)
<b>DISPLAY RANGE</b>	0 – 9999 SEC.
<b>ACCURACY</b>	+/- 1 SEC.
<b>OPERATING TEMPERATURE</b>	0 TO 50 °C.
<b>SIZE</b>	96 * 192 * 200 MM

## **CHAPTER 3**

### **PRINCIPLE OF OPERATION:**

1. WHEN THE INSTRUMENT IS POWERED ON, THE TIMER SHOWS "0000" IN "W-1" AND "----" IN "W-2".

ON RECEIVING PULSE FROM LIMIT SWITCH TIMER STAGE-1 STARTS AND RELAY-1 IS PUT "ON". THE "W-1" WILL INDICATE ON-TIME-1 & THE "W-2" WILL DISPLAY "ON\_1" & 1<sup>ST</sup> RELAY IS TURNED ON. THIS IS ON-TIMER MODE FOR 1<sup>ST</sup> RELAY. THE FIRST AMBER LED IS TURNED ON FOR VISUAL INDICATION.

2. AT THE COMPLETION OF THE 1<sup>ST</sup> ON-TIME, THE 1<sup>ST</sup> RELAY IS TURNED OFF & THE TIMER STOPS INDICATIONG "0000" IN "W-1" AND "----" IN "W-2". ON RECEIVING NEXT PULSE FROM LIMIT SWITCH STAGE-2 STARTS AND RELAY-2 IS PUT "ON". THE "W-1" WILL INDICATE ON-TIME-2 & THE "W-2" WILL DISPLAY "ON\_2" & 2<sup>ND</sup> RELAY IS TURNED ON. THIS IS ON-TIMER MODE FOR 2<sup>ND</sup> RELAY. THE SECOND AMBER LED IS TURNED ON FOR VISUAL INDICATION.

3. LIKEWISE THE INSTRUMENT WILL GO ON FOR THE REMAINING STAGES UPTO STAGE-8.

6. AT THE COMPLETION OF THE 8<sup>TH</sup> ON-TIME, THE INSTRUMENT WILL LOOP BACK TO STEP 1<sup>ST</sup> ON-TIME STAGE i.e. TURNING ON THE 1<sup>ST</sup> RELAY.

THIS IS HOW THE TIMER WILL WORK.

7. RESET KEY IS PROVIDED TO RESET THE TIMER AND START FROM THE FIRST STAGE ON-TIME ON RECEIVING PULSE FROM LIMIT SWITCH.

**NOTE:**

IF ON TIME OF ANY STAGE IS "ZERO". THEN TIMER WILL GOTO THE NEXT STAGE.

## **CHAPTER 4**

### **KEYBOARD SETTINGS:**

#### **TO SET SETPOINTS FOR INDIVIDUAL RELAYS**

KEYS	DISPLAY	COMMENT
PRESS SET	0010 SP_1	LAST SET VALUE VIZ. 0010 SECONDS. THIS IS THE TIME FOR WHICH THE 1 <sup>ST</sup> RELAY WILL REMAIN ON.
ARROW KEYS		TO CHANGE THE TIME.
ENT	0010 SP_2	LAST SET VALUE VIZ. 0010 SECONDS. THIS IS THE TIME FOR WHICH THE 2 <sup>ND</sup> RELAY WILL REMAIN ON.
ARROW KEYS		TO CHANGE THE TIME.

SIMILAR PROCEDURE IS APPLIED FOR REMAINING STAGES UPTO 8<sup>TH</sup>. AFTER SETTING 8<sup>TH</sup> STAGE ON-TIME, PRESS "ENT" TO COME OUT OF THE SETTING MODE.


AFTER THIS LAST STEP THE TIMER WILL RESUME THE COUNTING.

**NOTE:**

ALWAYS REMEMBER TO COME OUT OF THE KEYBOARD SETTING MODE.

## CHAPTER 5

### CONNECTION DIAGRAM:

<i>Nippon Technologies</i> 106, Shivsagar Ind Estate, Opp. Kotkar Industries, Kotkar Road, Goregaon – East, Mumbai – 400 063 Tel.: 91-22-29276841 / 29271050      E-mail: nipponitech@vsnl.com   * www.nipponinstruments.com																																																															
MODEL No. : <u>4008u</u>					SR No : <u>02160432</u>																																																										
INPUT TYPE : <u>DI</u>					ID No : <u>ID.0339/1215</u>																																																										
<table border="1" style="margin: auto; border-collapse: collapse;"> <tr> <th colspan="3" style="padding: 5px;">DI</th> </tr> <tr> <td style="padding: 5px;">+ 24V</td> <td style="padding: 5px;">IN</td> <td style="padding: 5px;">ORG</td> </tr> </table>										DI			+ 24V	IN	ORG																																																
DI																																																															
+ 24V	IN	ORG																																																													
<table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <tr> <th colspan="3" style="padding: 5px;">POWER 230 Vac</th> <th colspan="3" style="padding: 5px;">Relay-1</th> <th colspan="3" style="padding: 5px;">Relay-2</th> <th colspan="3" style="padding: 5px;">Relay-3</th> <th colspan="3" style="padding: 5px;">Relay-4</th> <th colspan="3" style="padding: 5px;">Relay-5</th> <th colspan="3" style="padding: 5px;">Relay-6</th> <th colspan="3" style="padding: 5px;">Relay-7</th> <th colspan="3" style="padding: 5px;">Relay-8</th> </tr> <tr> <td style="padding: 5px;">P</td> <td style="padding: 5px;">N</td> <td style="padding: 5px;">E</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> <td style="padding: 5px;">NC</td> <td style="padding: 5px;">C</td> <td style="padding: 5px;">NO</td> </tr> </table>										POWER 230 Vac			Relay-1			Relay-2			Relay-3			Relay-4			Relay-5			Relay-6			Relay-7			Relay-8			P	N	E	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO
POWER 230 Vac			Relay-1			Relay-2			Relay-3			Relay-4			Relay-5			Relay-6			Relay-7			Relay-8																																							
P	N	E	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO	NC	C	NO																																					

<div><div></div><div><div></div><div></div><div></div></div></div>									
<div><div>P N E</div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>	<div><div></div><div><div></div><div></div><div></div></div></div>